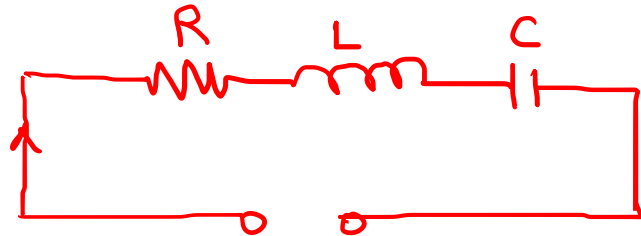


## Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

⇒ Series R-L-C circuit



$$(V = V_m \sin \omega t), \omega \uparrow$$

$$X_L = \omega L = 2\pi fL \quad f=0, X_L=0, f=\infty, X_L=\infty$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} \quad f=0, X_C=\infty, f=\infty, X_C=0$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

at some frequency ( $f_r$ )

$$X_L = X_C$$


$$Z = R + j(X_L - X_C) = R$$

Frequency at which  $X_L = X_C$  is called resonant frequency.

# Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

⇒ Series R-L-C circuit

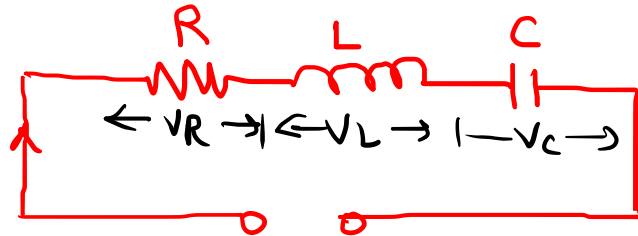

$$(V = V_m \sin \omega t), \omega \uparrow$$

$$\text{At } f = f_r \quad X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$


$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}} \quad \text{Hz}$$

$$2\pi f_r = 2\pi \cdot \frac{1}{2\pi \sqrt{LC}}$$

$$\omega_r = \frac{1}{\sqrt{LC}} \quad \text{rad/sec.}$$

phasor diagram at  $f = f_r$ .

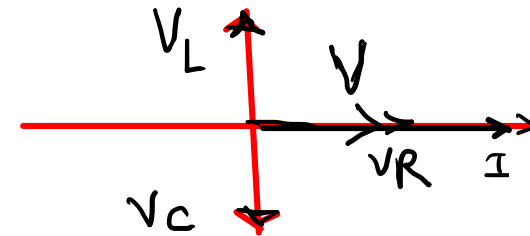



$$V_L = V_C$$

$$\text{PF} = \cos \phi = 1$$

$$\phi = 0$$
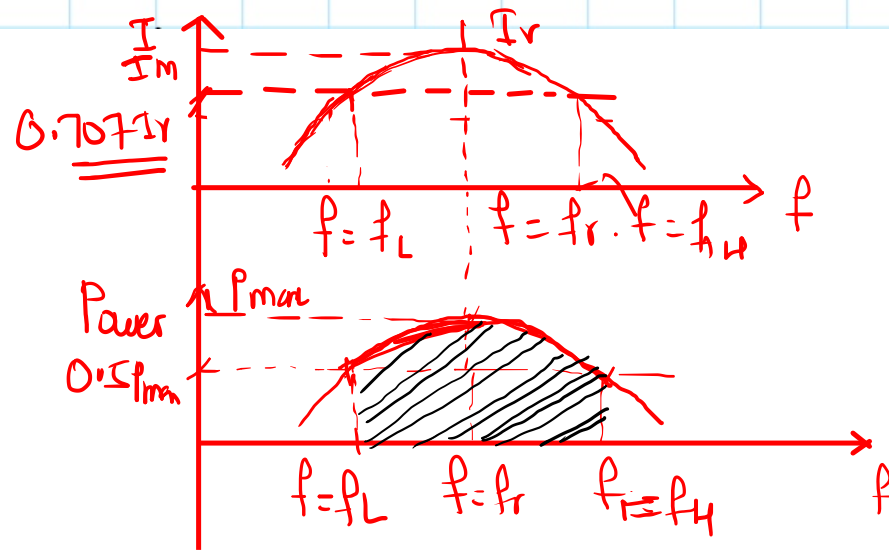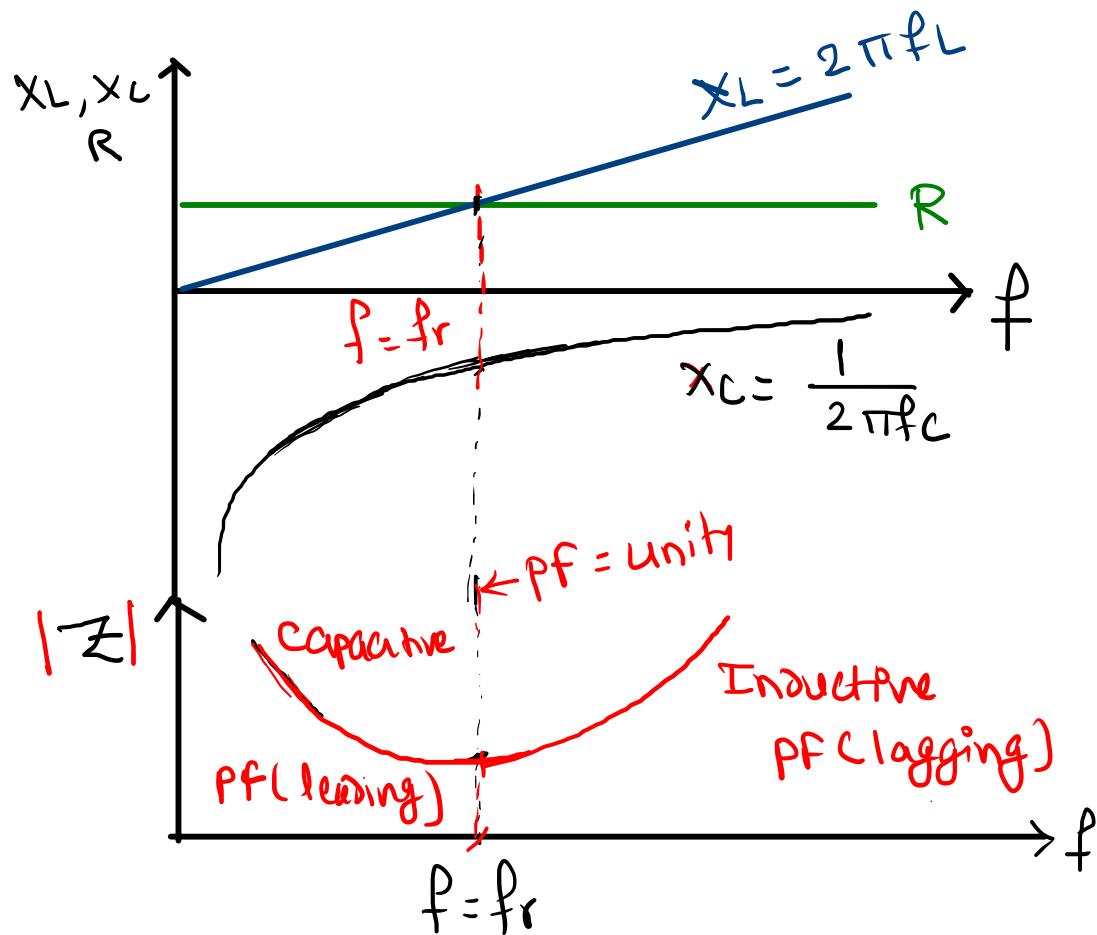
# Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.



$$BW = f_H - f_L \Rightarrow \text{Bandwidth.}$$

$f_L \rightarrow$  Lower cut-off freq<sup>n</sup>

$f_H \rightarrow$  Higher cut-off freq<sup>n</sup>.

$f_L, f_H$  are half power frequencies

$$P = I_r^2 R \quad \text{at } f = f_r \quad I = I_r$$

$$P_r = I_r^2 R$$

$$\frac{P_r}{2} = \frac{I_r^2 R}{2} = \left( \frac{I_r}{\sqrt{2}} \right)^2 R = (0.707 I_r)^2 R$$

## Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

⇒ R-L-C series resonance circuit is called acceptor circuit  
at  $f = f_r$   $I = I_r \rightarrow$  maximum.

⇒ voltage magnification circuit :

$$X_L = X_C \quad I = I_r \rightarrow \text{maximum} = \frac{V}{R}$$

$$I_r \cdot X_L = I_r \cdot X_C$$

$$|V_L| = |V_C| > \text{applied voltage (V)}$$

$$V_L = I_r \cdot X_L = \frac{V}{R} \omega_r L = \frac{V}{R} \cdot \frac{1}{\sqrt{LC}} \cdot L = \frac{V}{R} \sqrt{\frac{L}{C}}$$

$$V_C = I_r \cdot X_C = \frac{V}{R} \cdot \frac{1}{\omega_r C} = \frac{V}{R} \cdot \frac{\sqrt{LC}}{C} = \frac{V}{R} \cdot \sqrt{\frac{LC}{C^2}} = \frac{V}{R} \sqrt{\frac{L}{C}}$$

## Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

$$\text{At } f = f_r, \omega R = \omega r \quad (V_L = V_C) > V$$

$$V_C = I X_C \quad \text{or} \quad V_L = I X_L$$

$$Z = R + j(X_L - X_C)$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V_C = I \cdot X_C = \frac{V}{Z} \cdot X_C = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \cdot X_C$$

$$V_C = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cdot \frac{1}{\omega C}$$

squaring both sides

$$V_C^2 = \frac{V^2}{[R^2 + (\omega L - \frac{1}{\omega C})^2] \omega^2 C^2}$$

$$V_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2 \omega^2 C^2}$$

$$V_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2}$$

$$\frac{dV_C^2}{d\omega} = 0$$

## Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

$$\hat{V}_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2 \omega^2 C^2}$$

$$V_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2}$$

$$\frac{dV_C^2}{d\omega} = 0$$

$$0 = \frac{0 - V^2 (2\omega R^2 C^2 + 2(\omega^2 LC - 1) \cdot 2\omega LC)}{[\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2]^2}$$

$$V \neq 0,$$

$$2\omega R^2 C^2 + 2(\omega^2 LC - 1) \cdot 2\omega LC = 0$$

$$2\omega C [R^2 C + 2(\omega^2 LC - 1)L] = 0$$

$$\omega \neq 0 \quad C \neq 0$$

$$R^2 C + 2\omega^2 LC - 2L = 0$$

$$2\omega^2 LC = 2L - R^2 C$$

$$\omega^2 = \frac{\cancel{2L}}{2L^2 C} - \frac{R^2 \cancel{C}}{2L^2 \cancel{C}}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\frac{R^2}{2L^2} \ll \frac{1}{LC}$$

$$\omega^2 = \frac{1}{LC} \quad \& \quad \omega = \frac{1}{\sqrt{LC}} = \omega_r$$

# Resonance

Resonance is said to occur when the current is either maximum or minimum for a particular frequency of the AC input. At resonance circuit impedance becomes minimum or maximum. The power factor of the circuit becomes unity.

$$\hat{V}_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2 \omega^2 C^2}$$

$$V_C^2 = \frac{V^2}{\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2}$$

$$\frac{dV_C^2}{d\omega} = 0$$

$$0 = \frac{0 - V^2 (2\omega R^2 C^2 + 2(\omega^2 LC - 1) \cdot 2\omega LC)}{[\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2]^2}$$

$$V \neq 0,$$

$$2\omega R^2 C^2 + 2(\omega^2 LC - 1) \cdot 2\omega LC = 0$$

$$2\omega C [R^2 C + 2(\omega^2 LC - 1)L] = 0$$

$$\omega \neq 0 \quad C \neq 0$$

$$R^2 C + 2\omega^2 LC - 2L = 0$$

$$2\omega^2 LC = 2L - R^2 C$$

$$\omega^2 = \frac{\cancel{2L}}{2L^2 C} - \frac{R^2 \cancel{C}}{2L^2 \cancel{C}}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\frac{R^2}{2L^2} \ll \frac{1}{LC}$$

$$\omega^2 = \frac{1}{LC} \quad \& \quad \omega = \frac{1}{\sqrt{LC}} = \omega_r$$

⇒ Bandwidth of R-L-C series resonant circuit

$$\Rightarrow I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \text{--- (1)}$$

at resonance  $I = I_r$   $P = P_r$  (maximum)

$$\text{at half power } I = \frac{I_r}{\sqrt{2}} = \frac{V}{R\sqrt{2}} \quad \text{--- (2)}$$

Substitute  $I$  in eqn (1)

$$\frac{\cancel{V}}{R\sqrt{2}} = \frac{\cancel{V}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\sqrt{2} \cdot R = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$



⇒ Bandwidth of R-L-C series resonant circuit

$$\sqrt{2} \cdot R = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

Squaring both sides

$$2R^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

Square root

$$\left(\omega L - \frac{1}{\omega C}\right) = \pm R$$

$$\left(\omega L - \frac{1}{\omega C}\right) = \pm R$$

$$\frac{\omega^2 LC - 1}{\omega C} = \pm R$$

$$\omega^2 LC - 1 = \pm R \cdot \omega C$$

$$\omega^2 LC \mp \omega RC - 1 = 0$$

$$\omega^2 \mp \omega \frac{R}{L} - \frac{1}{LC} = 0$$

finding roots of quadratic equation

$$\omega_1, \omega_2 = \frac{\pm \frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}}{2}$$

$$\omega_1, \omega_2 = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\frac{R^2}{4L^2} \ll \frac{1}{LC}$$

$$ax^2 + bx + c$$

$$x_1, x_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

⇒ Bandwidth of R-L-C series resonant circuit

$$\omega_1, \omega_2 = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\frac{R^2}{4L^2} \ll \frac{1}{LC}$$

$$\omega_1, \omega_2 = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}}$$

$$\omega_1, \omega_2 = \pm \frac{R}{2L} \pm \omega_r$$

Since  $\omega_r$  cannot be negative

$$\omega_1, \omega_2 = \omega_r \pm \frac{R}{2L}$$

$$\omega_1 = \omega_L = \omega_r - \frac{R}{2L}$$

$$\omega_2 = \omega_H = \omega_r + \frac{R}{2L}$$

$$BW = \omega_H - \omega_L$$

$$= \cancel{\omega_r} + \frac{R}{2L} - \cancel{\omega_r} + \frac{R}{2L}$$

$$BW = 2 \cdot \frac{R}{2L}$$

$$BW = \frac{R}{L} \text{ rad/sec}$$

## ⇒ Quality Factor (Q)

$$Q = \frac{\text{Potential drop across } L/C \text{ at resonance}}{\text{Potential drop across } R \text{ at resonance.}}$$

$$Q = \frac{I_r \times X_L \text{ OR } I_r \times X_C}{I_r \times R}$$

$$Q = \frac{X_L}{R} \text{ OR } \frac{X_C}{R}$$

$$Q = \frac{\omega_r \cdot L}{R} \text{ OR } \frac{1}{\omega_r \cdot C \cdot R}$$

$$\omega_r = \frac{1}{\sqrt{LC}} \text{ OR } \frac{\sqrt{LC}}{\sqrt{C^2} \cdot R}$$

$$Q = \frac{1}{\sqrt{LC}} \sqrt{\frac{L^2}{R}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{OR } \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \omega_r \cdot \frac{L}{R}$$


$$\therefore \frac{R}{L} = BW.$$

$$Q = \left( \frac{\omega_r}{BW} \right) \frac{\text{rad/sec}}{\text{rad/sec}}$$

$$Q = \frac{2\pi f_r}{2\pi(BW)} = \frac{f_r}{BW} \left( \frac{\text{Hz}}{\text{Hz}} \right)$$

$$Q = \frac{f_r}{BW}$$

⇒ Quality Factor (Q) & BW.

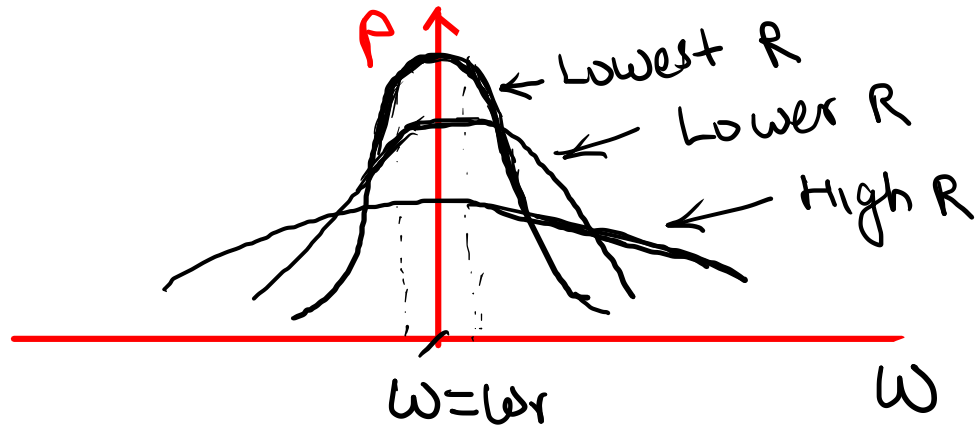

$$Q = \frac{X_L}{R} \quad R \uparrow \quad Q \downarrow$$


$$Q = \frac{W_r}{BW}$$

$$BW = \frac{W_r}{Q} \quad \uparrow$$

→ Low R → high quality factor Q, Sharp Bandwidth

→ Circuit is selective

⇒ Parallel Resonance.

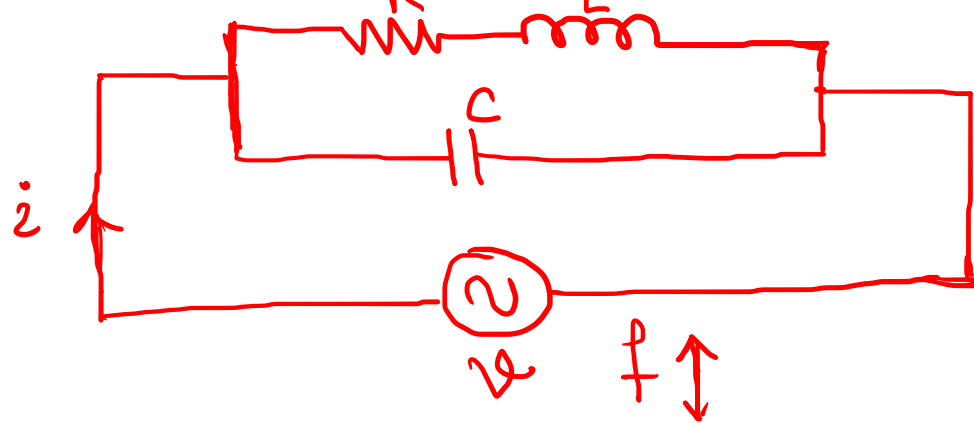

$$Z_1 = R + jX_L$$

$$Z_2 = -jX_C$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} = \frac{R - jX_L}{R^2 + X_L^2}$$

$$Y_2 = \frac{1}{-jX_C} = \frac{j}{X_C}$$

$$Y = Y_1 + Y_2$$

$$Y = \frac{R - jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$Y = \frac{R}{R^2 + X_L^2} - j \left[ \frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} \right]$$


For resonance reactive term must be zero.

$$\therefore \frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} = 0$$

$$\frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

$$X_L \cdot X_C = R^2 + X_L^2 \quad \text{--- (1)}$$

⇒ Parallel R Resonance.

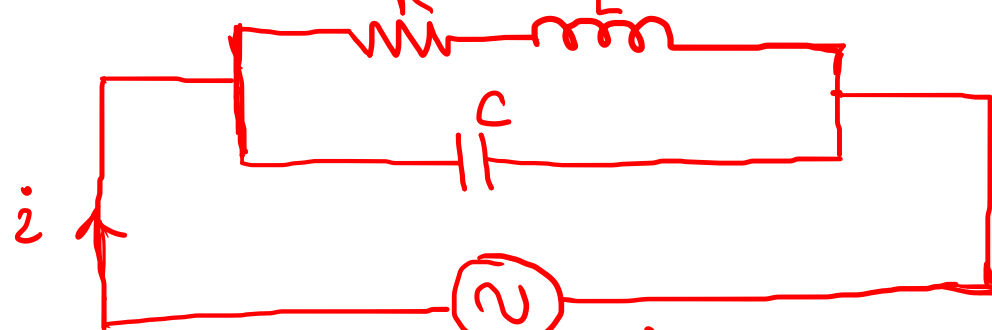

$$X_L \cdot X_C = R^2 + X_L^2 \quad \text{--- (1)}$$

At  $\omega = \omega_r$ .

$$\cancel{\omega_r} \cdot L \cdot \frac{1}{\cancel{\omega_r} \cdot C} = R^2 + (\omega_r L)^2$$

$$\frac{L}{C} = R^2 + \omega_r^2 L^2$$

$$\omega_r^2 L^2 = \frac{L}{C} - R^2$$

$$\omega_r^2 = \frac{1}{L \cdot C} - \frac{R^2}{L^2}$$


$$\omega_r^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\frac{R^2}{L^2} \ll \frac{1}{LC}$$


$$\therefore \omega_r = \frac{1}{\sqrt{LC}}$$

⇒ Parallel Resonance.

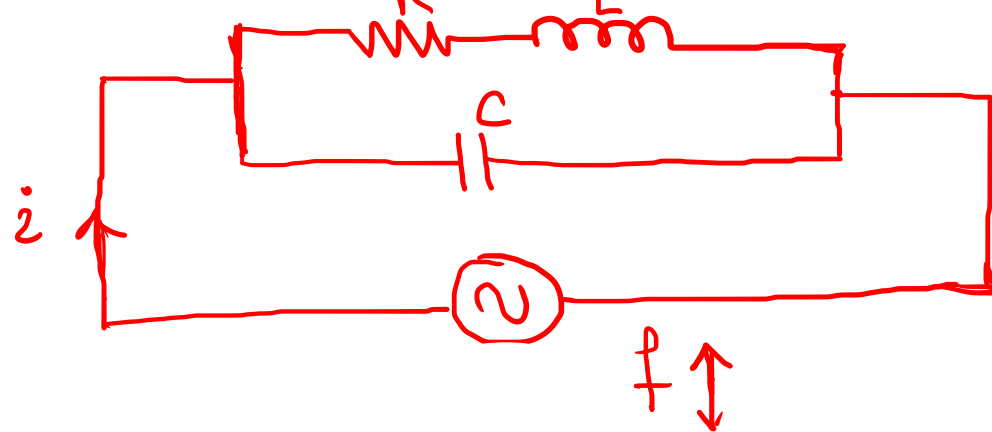


→ in parallel resonance circuit  
Admittance is minimum

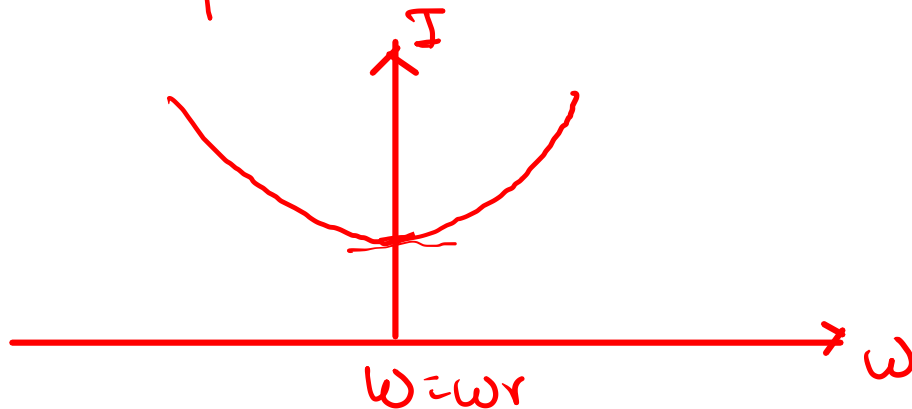$Z = \frac{1}{Y} \Rightarrow$  maximum. So  $I$  is minimum. So parallel resonant  
circuit rejects circuit.



⇒ Parallel R Resonance.

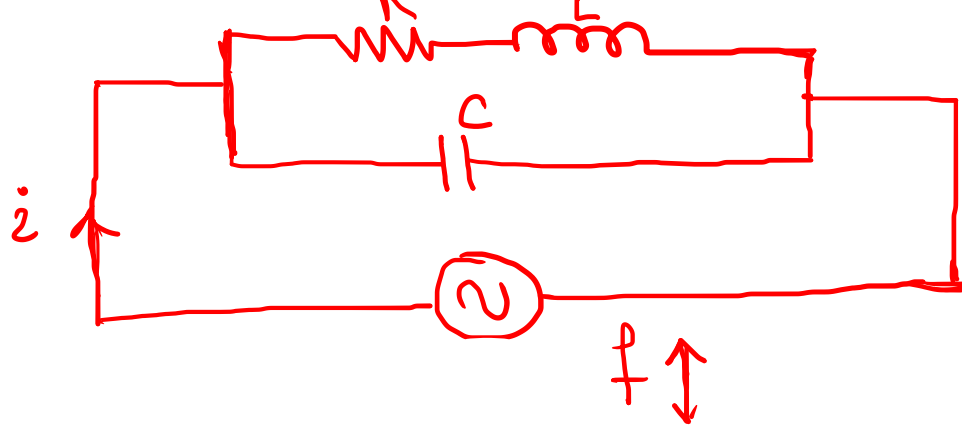

⇒ Impedance at resonance

$$Y = \frac{R}{R^2 + X_L^2} - j \left[ \frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} \right]$$

at resonance  $Y = \frac{R}{R^2 + X_L^2}$

impedance  $Z = \frac{1}{Y} = \frac{R^2 + X_L^2}{R}$

From equation (1)

$$R^2 + X_L^2 = X_L \cdot X_C$$

$$Z = \frac{X_L \cdot X_C}{R}$$

$$Z = \frac{\cancel{L\omega} \cdot L \cdot \frac{1}{\cancel{L\omega} \cdot C}}{R}$$

$$\boxed{Z = \frac{L}{CR}}$$

dynamic impedance of parallel resonant circuit.




## ⇒ Comparison of series / parallel resonant circuit

Parameter	series resonance	parallel Resonance.
Current	$I = \frac{V}{R}$ (maximum)	$I = \frac{V}{Z_D}$ (minimum)
Impedance	$Z = R$	$Z = Z_D = L/CR$
Power Factor	Unity (1)	Unity (1)
Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
Quality Factor	$Q = \frac{\omega_r L}{R}$	$Q = \frac{\omega_r \cdot L}{R}$
magnification	$(V_L, V_C) > V$ (voltage magn) Acceptor circuit	$(I_L, I_C) > I$ (current magn) Rejector circuit.

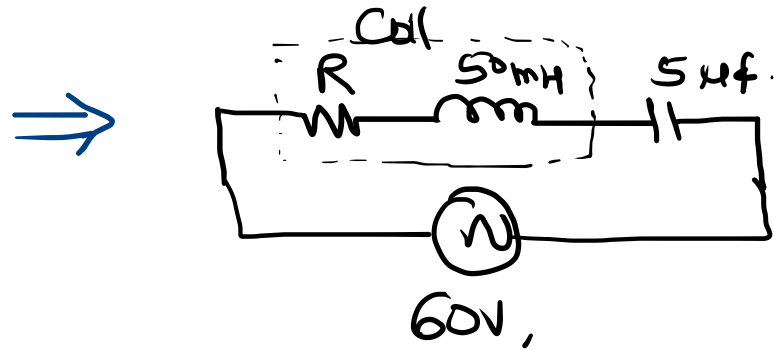Example

⇒ ①

A 5 μF capacitor is connected in series with the coil having an inductance of 50 mH. Calculate frequency of resonance & resistance of the coil if a 60V source operating at resonance causes current of 1.5 A. What is quality factor of coil?



at resonance  $Z = R$

$$\Rightarrow Z = R = \frac{60}{1.5} = 40 \Omega$$

$$\rightarrow f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{50 \times 10^{-3} \times 5 \times 10^{-6}}}$$

$$f_r = 318 \text{ Hz}$$

$$\Rightarrow Q = \frac{\omega_r L}{R}$$

$$Q = \frac{2\pi \times 318 \times 50 \times 10^{-3}}{40}$$


$$Q \approx 2.5$$

Example

⇒ ①

An non-inductive resistance of  $12\ \Omega$ , an inductance of  $0.2\ \text{H}$  & capacitor of  $9\ \mu\text{F}$  are connected in series. Calculate (i) current at resonance (ii) resonant frequency (iii) voltage across each component when a voltage of  $35\ \text{V}$  at resonance is applied to whole circuit.

⇒

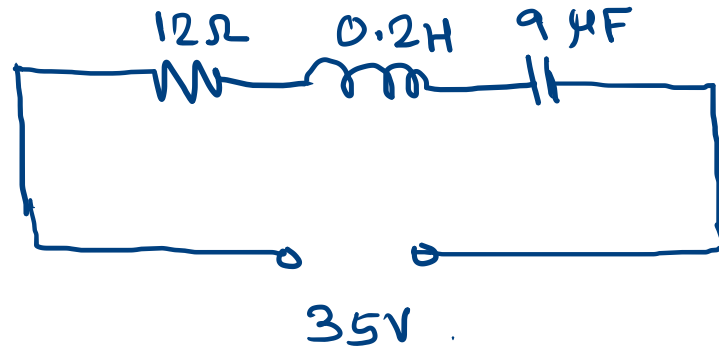

③

$$V_R = I_r \times R = 2.9 \times 12 = 34.8\ \text{V}$$

$$V_L = I_r \cdot X_L = 2.9 \times (2\pi \times 119 \times 0.2)$$

$$V_L = 433.65\ \text{V}$$

$$V_C = I_r \cdot X_C = 2.9 \times \frac{1}{2\pi \times 119 \times 9 \times 10^{-6}}$$

$$V_C = 430.95\ \text{V}$$

i) Current  $I_r = \frac{35}{12} = 2.9\ \text{A}$


ii) resonant freqn  $f_r = \frac{1}{2\pi\sqrt{LC}}$

$$f_r = \frac{1}{2\pi\sqrt{0.2 \times 9 \times 10^{-6}}} = 119\ \text{Hz}$$

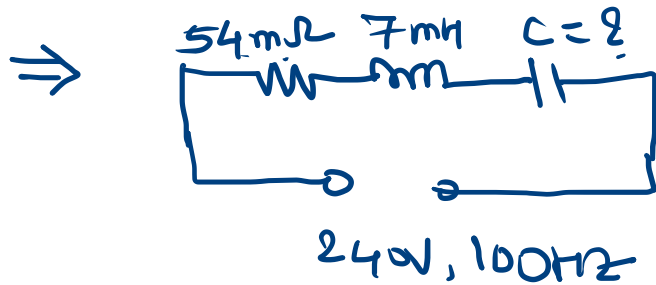Example



A series R-L-C circuit consisting of a coil & capacitor connected across 240V, 100Hz supply. If the coil has 54 mΩ resistance & 7 mH inductance. (i) Calculate value of capacitor at 100Hz resonant frequency (ii) Quality factor of the coil (iii) Half power frequencies



$$C = \frac{1}{4\pi^2 f_r^2 \times L} = \frac{1}{4\pi^2 (100)^2 \times 7 \times 10^{-3}}$$

$$C \approx 362 \mu\text{F}$$

(i) →  $f_r = 100 \text{ Hz}$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

(ii)  $Q = \frac{\omega_r L}{R} = \frac{2\pi \times 100 \times 7 \times 10^{-3}}{54 \times 10^{-3}} = 81.45$

(iii)  $f_L = f_r - \frac{R}{4\pi L} = 100 - \frac{54 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}} = 99.38 \text{ Hz}$


$$f_H = f_r + \frac{R}{4\pi L} = 100 + \frac{54 \times 10^{-3}}{4\pi \times 7 \times 10^{-3}} = 100.61 \text{ Hz}$$

$$BW = f_H - f_L = 100.61 - 99.38 = 1.23 \text{ Hz}$$

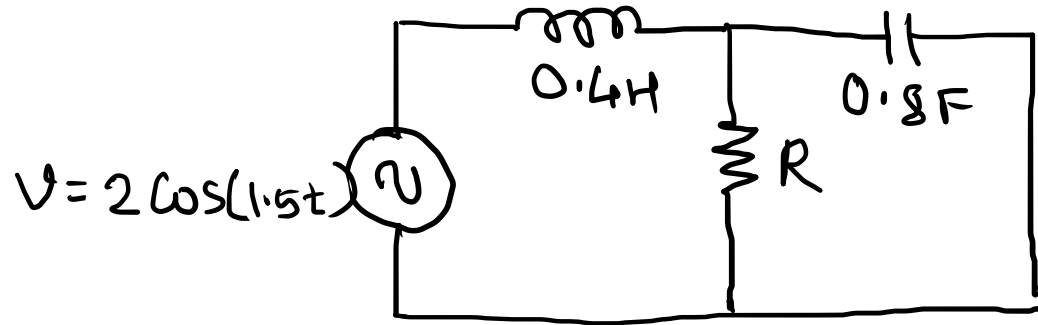Example

⇒ (iv)

Find value of R such that below circuit is at resonance.



⇒  $\omega = 1.5$   
Impedance  $(R || C) + X_L$

$$Z = jX_L + \left( \frac{R \times -jX_C}{R - jX_C} \right)$$

$$Z = (j1.5 \times 0.4) + \left( \frac{R \times \frac{1}{j(1.5 \times 0.8)}}{R + \left( \frac{1}{j1.5 \times 0.8} \right)} \right)$$

$$Z = j0.6 + \frac{R / j(1.2)}{R + \frac{1}{1.2j}}$$

$$Z = j0.6 + \frac{R}{1 + j1.2R}$$

$$Z = j0.6 + \frac{R(1 - j1.2R)}{1 + (1.2R)^2}$$

$$Z = \frac{R}{1 + (1.2R)^2} - j \left( \frac{1.2R^2}{1 + (1.2R)^2} - 0.6 \right)$$

At resonance reactive term = 0

$$\frac{1.2R^2}{1 + 1.44R^2} = 0.6$$

$$1.2R^2 = 0.6 + 0.864R^2$$


$$0.336R^2 = 0.6$$

$$R^2 = 1.78$$

$$\therefore R = 1.33 \Omega$$

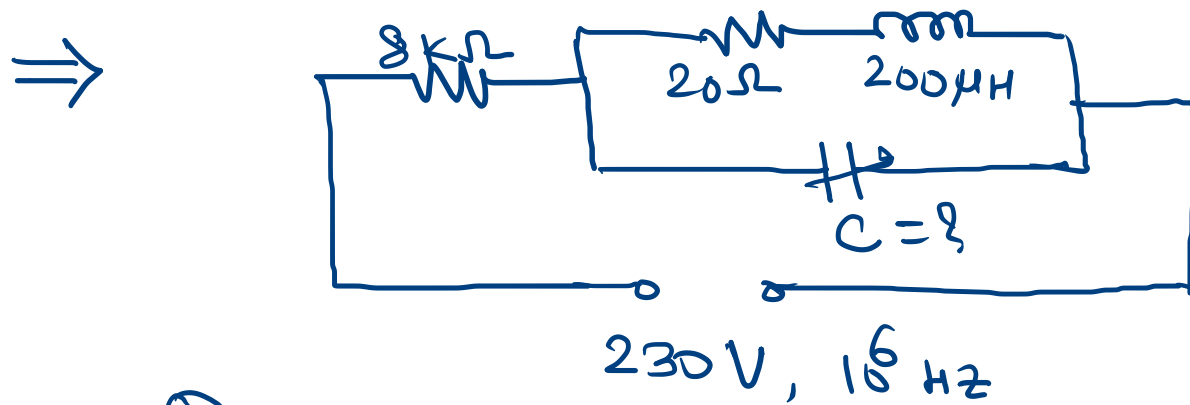Example

- ⇒ (v) In the following network find (i) value of capacitor  
(ii) quality factor (iii) impedance at resonance (iv) total current, if the circuit is at resonance.



⇒ (i)

$$f_r = 10^6$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f^2 = \frac{1}{4\pi^2} \left( \frac{1}{LC} - \frac{R^2}{L^2} \right)$$

$$(10^6)^2 = \frac{1}{4\pi^2} \left[ \frac{1}{200 \times 10^{-6} C} - \frac{20^2}{(200 \times 10^{-6})^2} \right]$$

$$C \approx 126.5 \text{ pF}$$

$$(ii) Q = \frac{2\pi f_r L}{R} \approx \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20}$$

(iii) Impedance at resonance ( $Z_T = 8k + Z_D$ )

$$Z_D = \frac{L}{CR} = \frac{200 \times 10^{-6}}{126.5 \times 10^{-12} \times 20}$$

$$Z_D = 78.74 \text{ k}\Omega$$

$$Z_T = 8 + 78.74 = 86.74 \text{ k}\Omega$$

$$(iv) I = \frac{230}{Z_T} = \frac{230}{86.74 \text{ k}} = 2.65 \text{ mA}$$